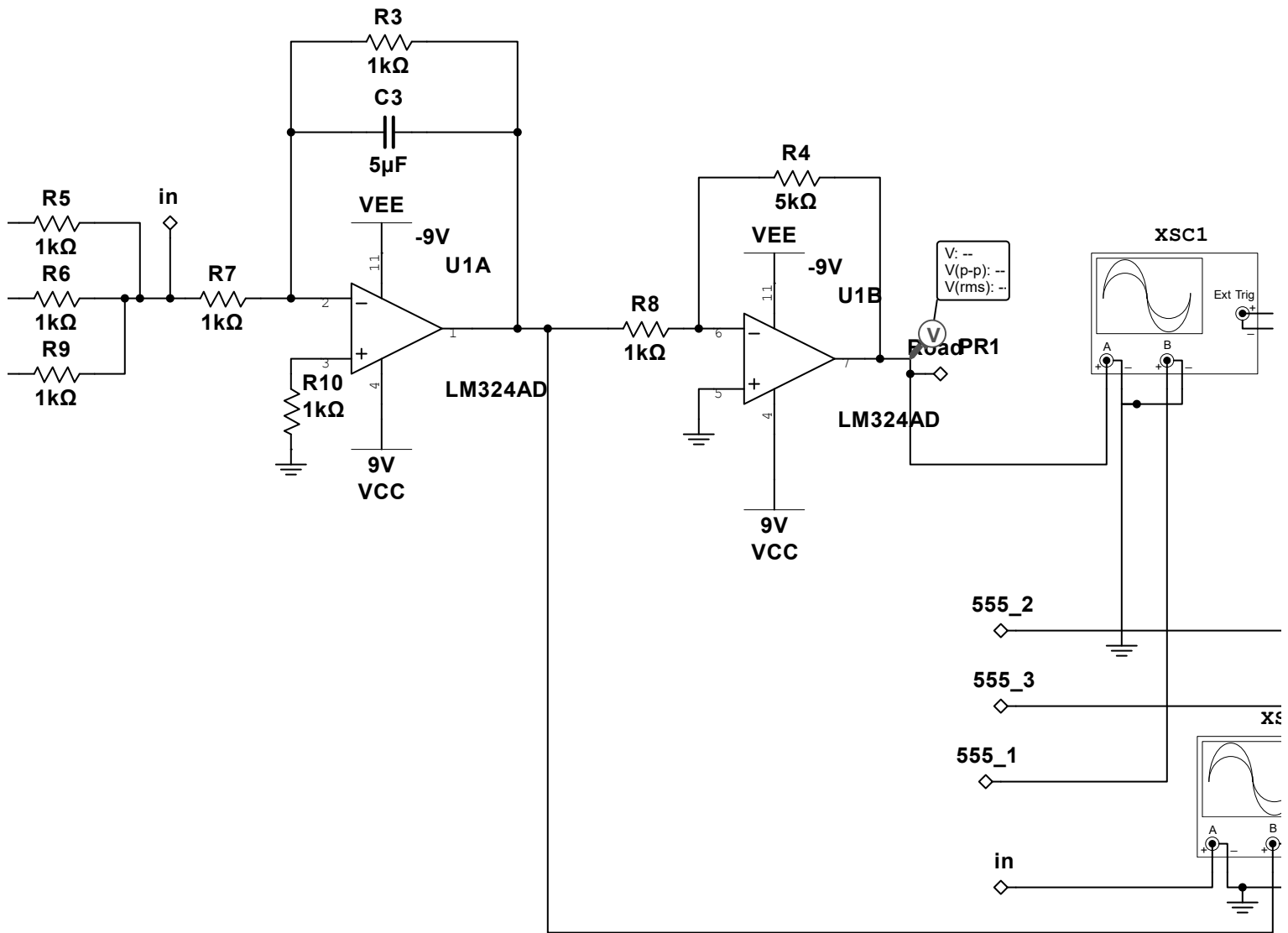


	8	9	10	11	12	13	14	15
--	---	---	----	----	----	----	----	----




The road circuit generates a windy path of voltages that can be shown on the road display circuit. This is create square waves generated with three 555 timer circuits. These signals are summed up into one input signal which integrator circuit. This integrator smooths out the input signal and outputs a windy path. This output signal is in inverting gain op amp with a gain of 5. This increases the output of the signal allowing it to be more readily dete display circuit.

The final generated road can be seen in oscilloscope XSC1.

Road Circuit

	16	17	18	19	20	21	22	
--	----	----	----	----	----	----	----	--

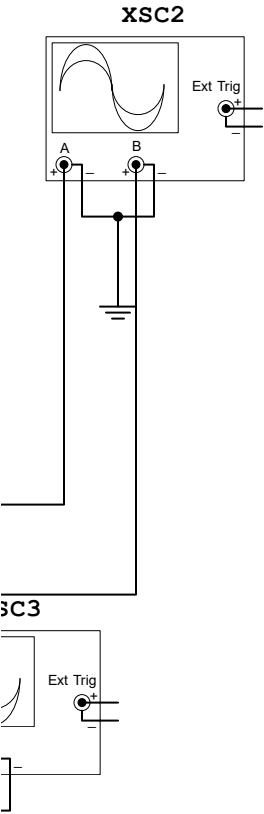

ed via 3 different
n is fed into an
putted into an
ected by the road

A
B
C
D
E
F
G
H
I
J

K

L

M

N

O

P

Q


R

S



T

U


Road Display

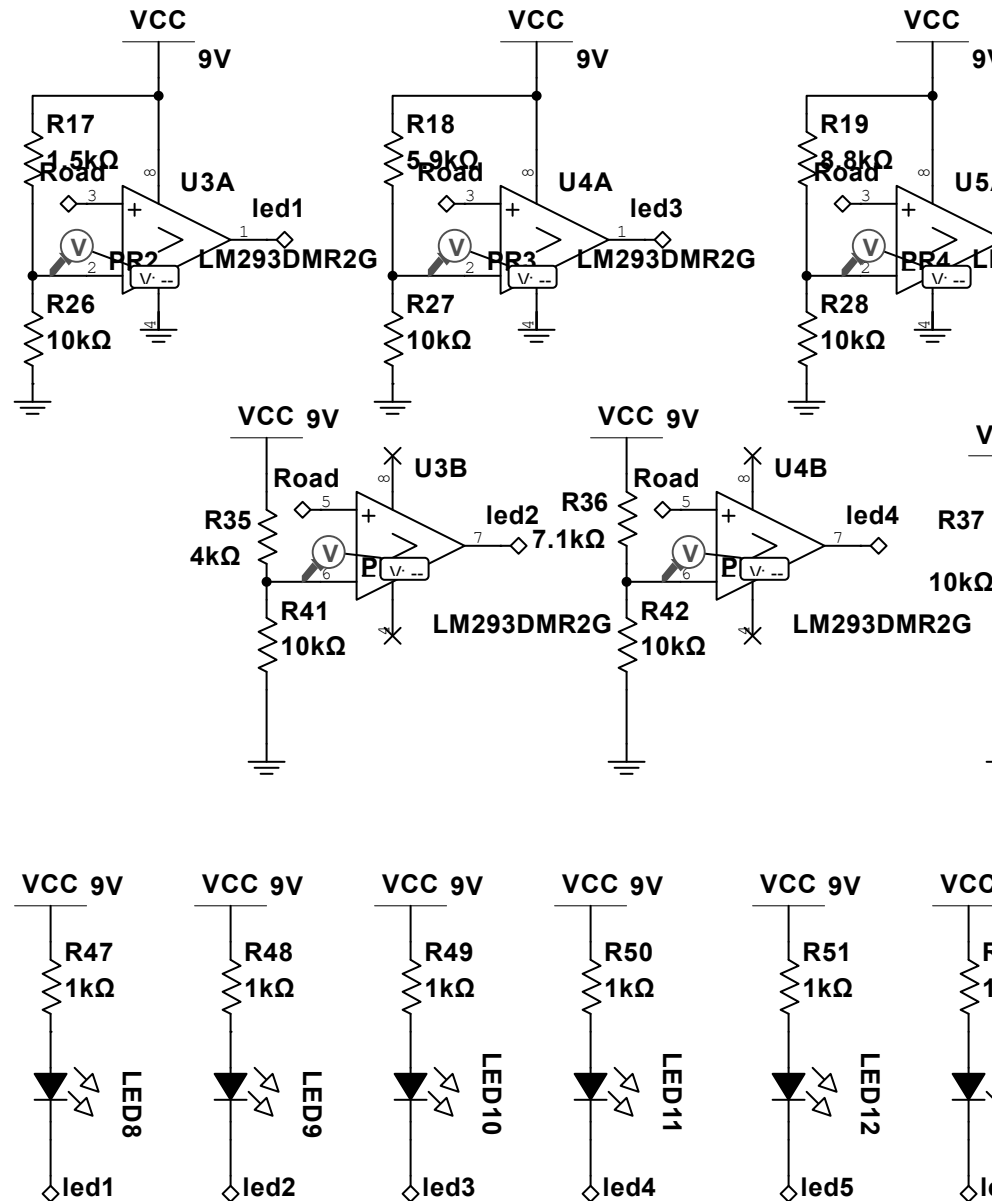

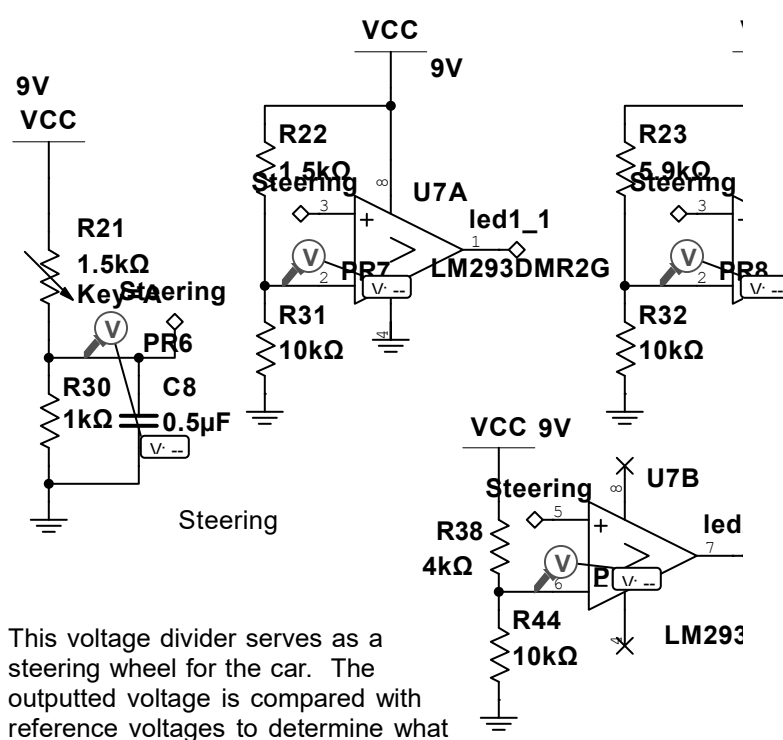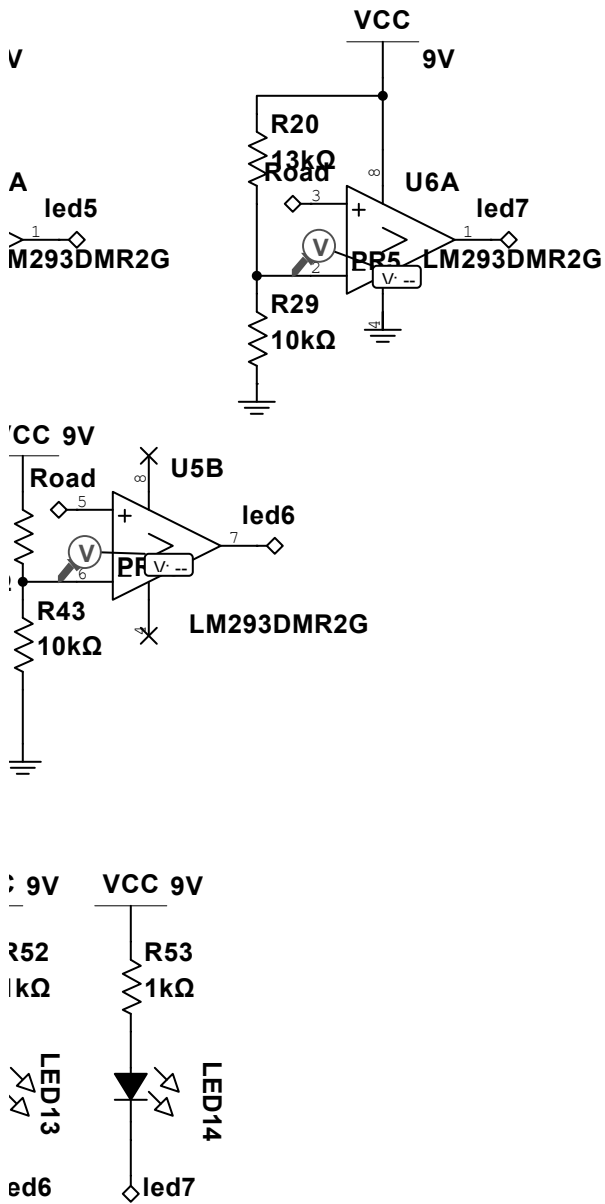The status circuit display what the difference between the road and If all of the lights are on, the car is on the road and is "winning." As drifting off of the road. Due to circuit lag and how much the road v and has a slow start up time when the simulation is turned on.



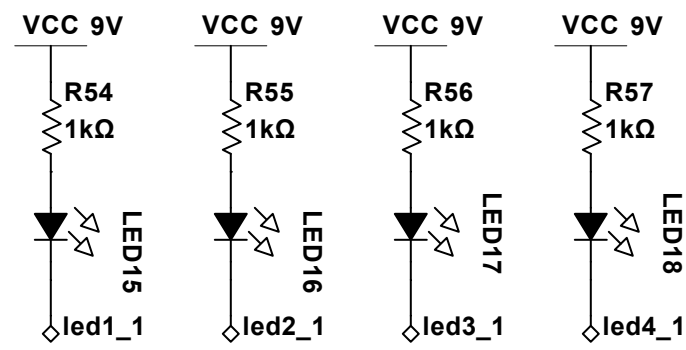This voltage divider serves as a steering wheel for the car. The outputted voltage is compared with reference voltages to determine what direction the car is pointing. The added capacitor serves as a lag feature to increase difficulty of steering.



The leds represent which direction the car is driving. If no all the way left. If all 7 leds are on, the car is pointing all the the car is driving straight forward.



The leds are separated from their respective comparators

Steering Wheel
100 %

the steering position is.
the lights turn off, the car is
varies this is not entirely accurate

Status


Steering



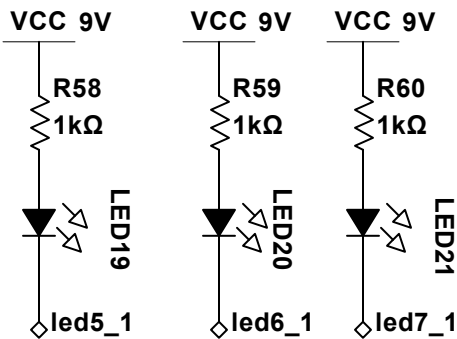
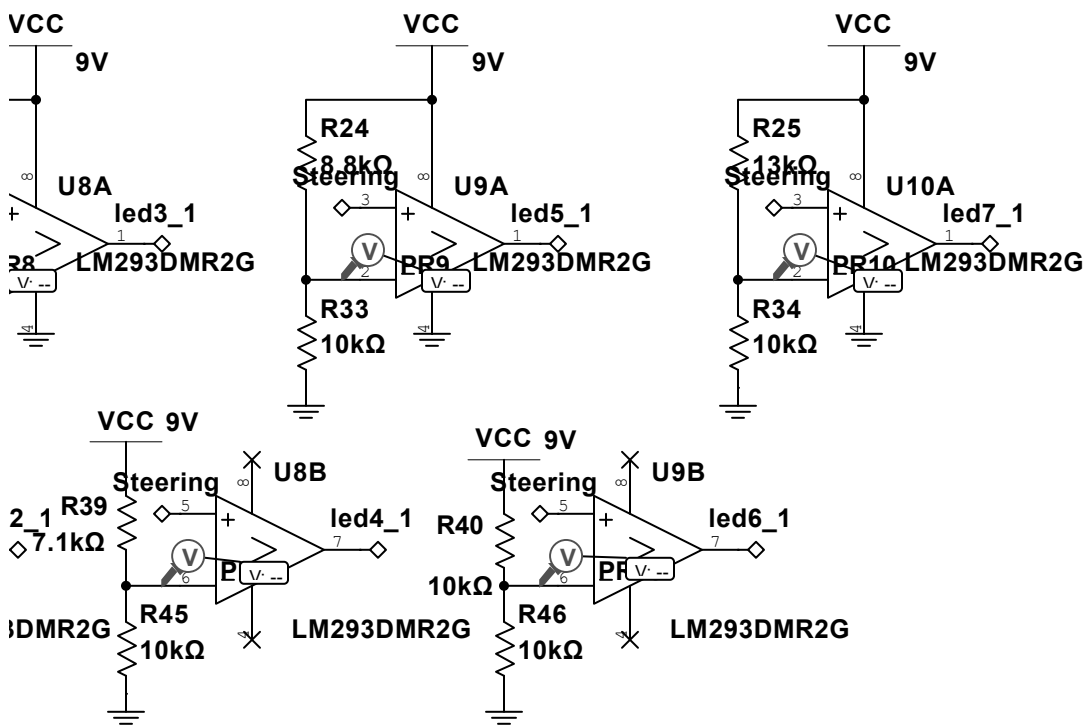


- 10% - led 1 on
- 30% - led 2 on
- 40% - led 3 on
- 50% - led 4 on
- 60% - led 5 on
- 70% - led 6 on
- 90% - led 7 on


leds are on, the car is pointing
e way right. If 4/7 leds are on,
ere to better illustrate this guage effect.

K
L
M
N
O
P
Q
R
S
T
U

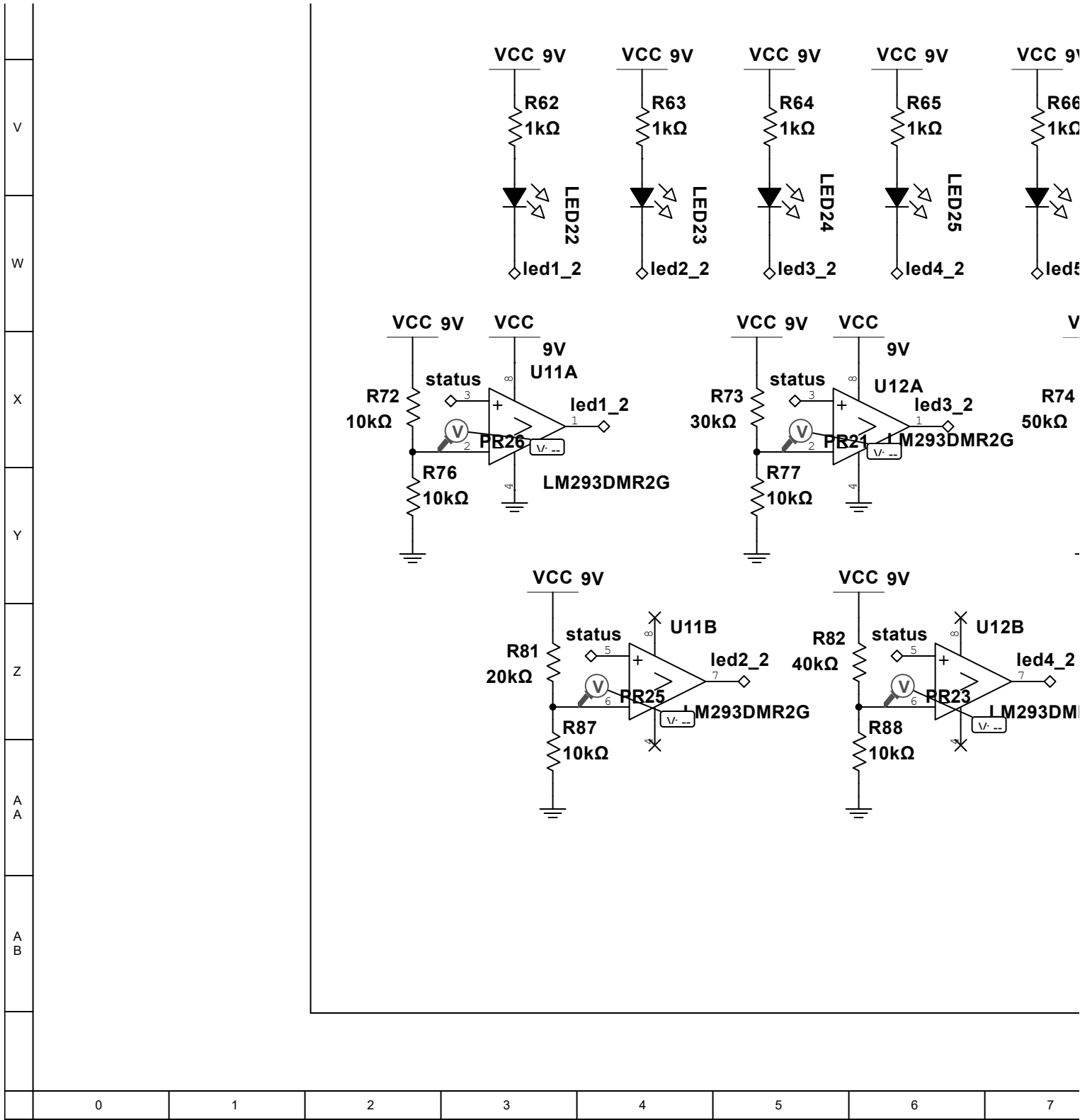

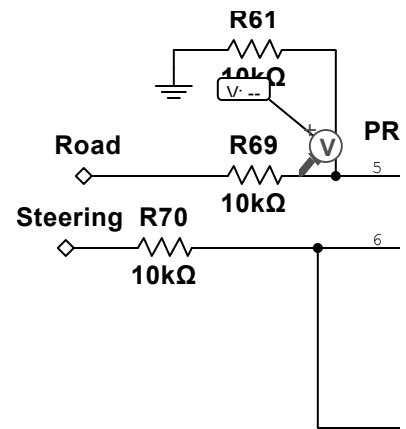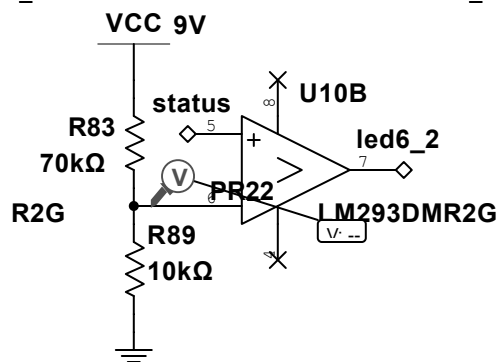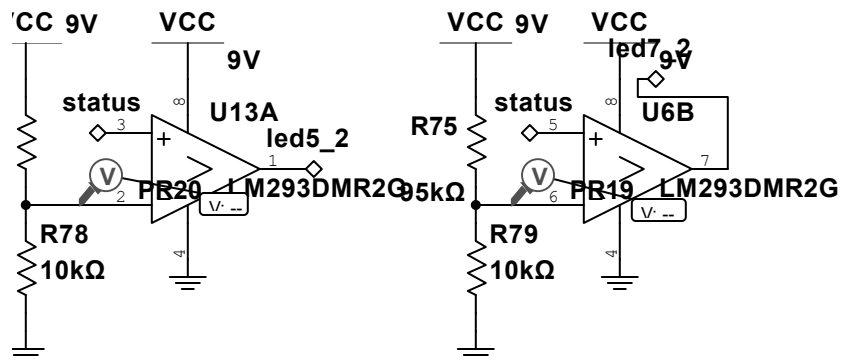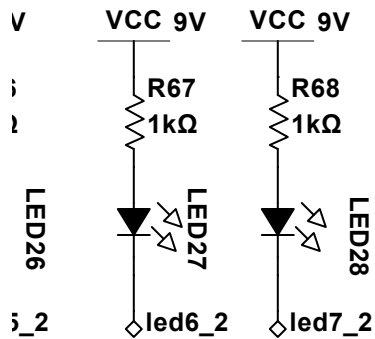


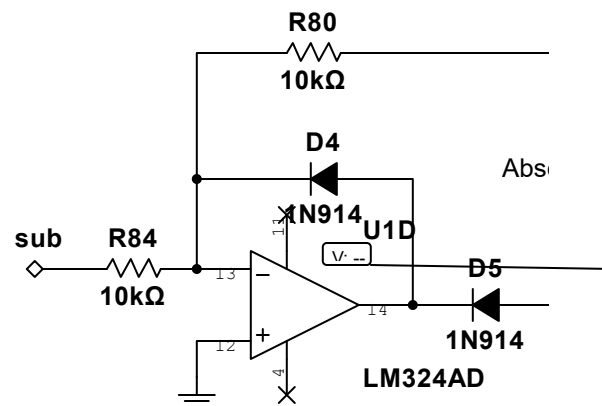A subtractor circuit to determine the dif
 $V_{out} = \text{Road} - \text{Steering}$




An absolute value circuit that performs the
 The output from this will be used to deter

	8	9	10	11	12	13	14	15
--	---	---	----	----	----	----	----	----

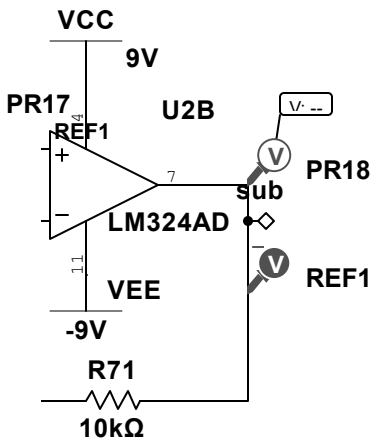

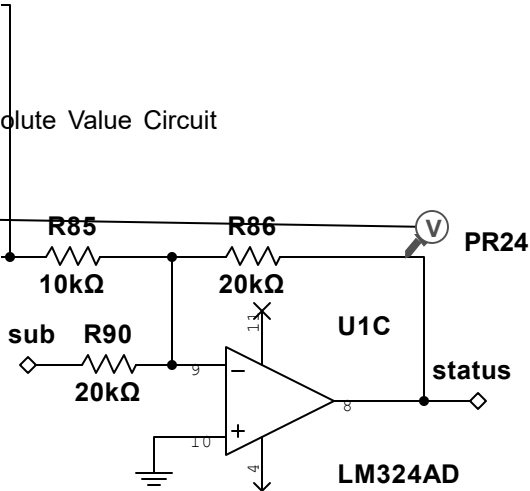ference between the road voltage and the steering voltage.



operation $V_{out} = |sub| = |Road - Steering|$
 nine how far from the intended direction the car is steering in (i.e. is it crashing).

	16	17	18	19	20	21	22	
--	----	----	----	----	----	----	----	--

V	
W	
X	
Y	
Z	
A A	
A B	